

# Intuitive Analog Circuit Design



# Intuitive Analog Circuit Design

*A Problem-Solving Approach  
using Design Case Studies*

*By*

***Marc T. Thompson, Ph.D.***



ELSEVIER

AMSTERDAM • BOSTON • HEIDELBERG • LONDON  
NEW YORK • OXFORD • PARIS • SAN DIEGO  
SAN FRANCISCO • SINGAPORE • SYDNEY • TOKYO

Newnes is an imprint of Elsevier



Newnes

Newnes is an imprint of Elsevier  
30 Corporate Drive, Suite 400, Burlington, MA 01803, USA  
Linacre House, Jordan Hill, Oxford OX2 8DP, UK

Copyright © 2006, Elsevier Inc. All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.

Permissions may be sought directly from Elsevier's Science & Technology Rights Department in Oxford, UK: phone: (+44) 1865 843830, fax: (+44) 1865 853333, e-mail: [permissions@elsevier.com.uk](mailto:permissions@elsevier.com.uk). You may also complete your request on-line via the Elsevier homepage (<http://elsevier.com>), by selecting "Customer Support" and then "Obtaining Permissions."



Recognizing the importance of preserving what has been written,  
Elsevier prints its books on acid-free paper whenever possible.

### Library of Congress Cataloging-in-Publication Data

Thompson, Marc T.

Intuitive analog circuit design.

p. cm.

ISBN-13: 978-0-7506-7786-8 (pbk. : alk. paper)

ISBN-10: 0-7506-7786-4 (pbk. : alk. paper) 1. Electronic circuit design.

I. Title.

TK7867.T48165 2006

621.3815--dc22

2005036750

### British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library.

ISBN-13: 978-0-7506-7786-8

ISBN-10: 0-7506-7786-4

For information on all Newnes publications  
visit our Web site at [www.books.elsevier.com](http://www.books.elsevier.com)

06 07 08 09 10 10 9 8 7 6 5 4 3 2 1

Printed in the United States of America

Working together to grow  
libraries in developing countries

[www.elsevier.com](http://www.elsevier.com) | [www.bookaid.org](http://www.bookaid.org) | [www.sabre.org](http://www.sabre.org)

ELSEVIER

BOOK AID  
International

Sabre Foundation

## **In memoriam**

To my mother, Minnie Ann Thompson,  
who bought me my first transistors when I was a child.

## **Dedication**

To Lisa and Sophie M., for your love and patience.  
The book is finally done. Mazel tov!



# Contents

|   |                 |
|---|-----------------|
| <b>Preface</b> .....  | <b><i>x</i></b> |
| <b>Chapter 1: Introduction and Motivation</b> .....   | <b>1</b>        |
| The Need for Analog Designers.....  | 1               |
| Some Early History of Technological Advances in Analog Integrated Circuits .....              | 2               |
| Digital vs. Analog Implementation: Designer's Choice .....                                    | 6               |
| So, Why Do We Become Analog Designers? .....  | 8               |
| Note on Nomenclature in this Text .....   | 9               |
| Note on Coverage in this Book.....  | 9               |
| References.....   | 10              |
| U.S. Patents.....   | 12              |
| <b>Chapter 2: Review of Signal-Processing Basics</b> .....                                    | <b>13</b>       |
| Review of Laplace Transforms, Transfer Functions and Pole-Zero Plots .....                    | 13              |
| First-Order System Response .....   | 15              |
| Second-Order Systems.....   | 23              |
| Review of Resonant Electrical Circuits .....  | 33              |
| Use of Energy Methods to Analyze Undamped Resonant Circuits .....                             | 34              |
| Transfer Functions, Pole/Zero Plots and Bode Plots .....                                      | 36              |
| Risetime for Cascaded Systems .....   | 37              |
| Chapter 2 Problems.....   | 38              |
| References.....   | 42              |
| <b>Chapter 3: Review of Diode Physics and the Ideal<br/>(and Later, Nonideal) Diode</b> ..... | <b>43</b>       |
| Current Flow in Insulators, Good Conductors and Semiconductors .....                          | 43              |
| Electrons and Holes .....   | 45              |
| Drift, Diffusion, Recombination and Generation.....   | 48              |
| Effects of Semiconductor Doping.....  | 53              |
| PN Junction Under Thermal Equilibrium .....   | 54              |
| PN Junction Under Applied Forward Bias.....   | 57              |

## Contents

---

|   |            |
|---|------------|
| Reverse Biased Diode .....  | 61         |
| Ideal Diode Equation .....  | 62         |
| Charge Storage in Diodes .....  | 63         |
| Charge Storage in the Diode Under Forward Bias .....  | 65         |
| Reverse Recovery in Bipolar Diodes .....  | 65         |
| Reverse Breakdown .....   | 66         |
| Taking a Look at a Diode Datasheet .....  | 67         |
| Some Quick Comments on Schottky Diodes .....  | 70         |
| Chapter 3 Problems .....  | 71         |
| References .....  | 74         |
| <b>Chapter 4: Bipolar Transistor Models .....</b>   | <b>75</b>  |
| A Little Bit of History .....   | 75         |
| Basic NPN Transistor .....  | 76         |
| Transistor Models in Different Operating Regions .....  | 79         |
| Low-Frequency Incremental Bipolar Transistor Model .....  | 82         |
| High-Frequency Incremental Model .....  | 85         |
| Reading a Transistor Datasheet .....  | 88         |
| Limitations of Hybrid-Pi Model .....  | 93         |
| Chapter 4 Problems .....  | 94         |
| References .....  | 95         |
| <b>Chapter 5: Basic Bipolar Transistor Amplifiers and Biasing .....</b>                                     | <b>97</b>  |
| The Issue of Transistor Biasing .....   | 97         |
| Some Transistor Amplifiers .....  | 101        |
| Chapter 5 Problems .....  | 121        |
| References .....  | 125        |
| <b>Chapter 6: Bandwidth Estimation Techniques and the<br/>  Method of Open-Circuit Time Constants .....</b> | <b>127</b> |
| Introduction to Open-Circuit Time Constants .....   | 127        |
| Transistor Amplifier Examples .....   | 132        |
| Chapter 6 Problems .....  | 156        |
| References .....  | 159        |
| <b>Chapter 7: Advanced Transistor Amplifier Techniques .....</b>  | <b>161</b> |
| Worst-Case Open-Circuit Time Constant Calculations .....  | 161        |
| High-Frequency Output and Input Impedance of Emitter-Follower Buffers .....                                 | 168        |
| Bootstrapping .....   | 177        |
| Short-Circuit Time Constants .....  | 184        |



---

|  |            |
|--|------------|
| Pole Splitting.....  | 196        |
| Chapter 7 Problems.....  | 202        |
| References.....  | 205        |
| <b>Chapter 8: High-Gain Bipolar Amplifiers and BJT Current Mirrors .....</b> | <b>207</b> |
| The Need to Augment the Hybrid-Pi Model.....                                 | 207        |
| Base-Width Modulation.....   | 209        |
| Finding Parameters from a Transistor Datasheet.....                          | 211        |
| Common-Emitter Amplifier with Current Source Load.....                       | 212        |
| Building Blocks.....   | 213        |
| Chapter 8 Problems.....  | 238        |
| References.....  | 240        |
| <b>Chapter 9: Introduction to MOSFET Devices and</b>                         |            |
| <b>Basic MOS Amplifiers .....</b>  | <b>241</b> |
| Some Early History of Field-Effect Transistors.....                          | 241        |
| Qualitative Discussion of Basic MOS Devices.....                             | 242        |
| Figuring Out the V/I Curve of a MOS Device.....                              | 243        |
| MOS Small-Signal Model (Low Frequency).....                                  | 246        |
| MOS Small-Signal Model (High Frequency).....                                 | 247        |
| Basic MOS Amplifiers.....  | 248        |
| Chapter 9 Problems.....  | 266        |
| References.....  | 268        |
| <b>Chapter 10: Bipolar Transistor Switching and the</b>                      |            |
| <b>Charge Control Model.....</b>   | <b>269</b> |
| Introduction.....  | 269        |
| Development of the Switching Models.....                                     | 269        |
| Reverse-Active Region.....   | 271        |
| Saturation.....  | 272        |
| Junction Capacitances.....   | 274        |
| Relationship Between Charge Control and Hybrid-Pi Parameters.....            | 274        |
| Finding Junction Capacitances from the Datasheet.....                        | 275        |
| Manufacturers' Testing.....  | 277        |
| Charge Control Model Examples.....   | 277        |
| Emitter Switching.....   | 292        |
| 2N2222 Datasheet Excerpts.....   | 294        |
| Chapter 10 Problems.....   | 298        |
| References.....  | 303        |

## Contents

---

|   |            |
|---|------------|
| <b>Chapter 11: Review of Feedback Systems.....</b>  | <b>305</b> |
| Introduction and Some Early History of Feedback Control .....                                   | 305        |
| Invention of the Negative Feedback Amplifier .....  | 306        |
| Control System Basics .....   | 308        |
| Loop Transmission and Disturbance Rejection .....   | 309        |
| Stability .....   | 310        |
| Routh Stability Criterion.....  | 311        |
| The Phase Margin and Gain Margin Tests .....  | 314        |
| Relationship Between Damping Ratio and Phase Margin.....  | 315        |
| Loop Compensation Techniques—Lead and Lag Networks .....  | 316        |
| Parenthetical Comment on Some Interesting Feedback Loops .....                                  | 317        |
| Appendix: MATLAB Scripts .....  | 338        |
| Chapter 11 Problems.....  | 342        |
| References.....   | 345        |
| <b>Chapter 12: Basic Operational Amplifier Topologies<br/>and a Case Study .....</b>            | <b>347</b> |
| Basic Device Operation .....  | 347        |
| Brief Review of LM741 Op-Amp Schematic .....  | 358        |
| Some Real-World Limitations of Operational Amplifiers .....                                     | 359        |
| Chapter 12 Problems.....  | 366        |
| References.....   | 367        |
| <b>Chapter 13: Review of Current Feedback Operational Amplifiers .....</b>                      | <b>369</b> |
| Conventional Voltage-Feedback Op-Amp and the<br>Constant “Gain Bandwidth Product” Paradigm..... | 369        |
| Slew Rate Limitations in Conventional Op-Amps.....  | 371        |
| Basic Current Feedback Op-Amp.....  | 372        |
| Absence of Slew Rate Limit in Current Feedback Op-Amps.....                                     | 375        |
| Manufacturer’s Datasheet Information for a Current Feedback Amplifier .....                     | 379        |
| A More Detailed Model and Some Comments on Current-Feedback<br>Op-Amp Limitations.....          | 381        |
| Chapter 13 Problems.....  | 382        |
| References.....   | 383        |
| <b>Chapter 14: Analog Low-Pass Filters.....</b>   | <b>385</b> |
| Introduction.....   | 385        |
| Review of Low-Pass Filter Basics .....  | 386        |
| Butterworth Filter.....   | 387        |
| Chebyshev Filter .....  | 390        |

---

|  |            |
|--|------------|
| Bessel Filter .....  | 395        |
| Comparison of Responses of Different Filter Types.....   | 398        |
| Filter Implementation.....   | 400        |
| Chapter 14 Problems.....   | 414        |
| References.....  | 416        |
| <b>Chapter 15: Review of Passive Components and a<br/>Case Study in PC Board Layout.....</b>   | <b>417</b> |
| Resistors.....   | 417        |
| Comments on Surface-Mount Resistors .....  | 419        |
| Comments on Resistor Types.....  | 420        |
| Capacitors .....   | 421        |
| Inductors .....  | 424        |
| Discussion of Printed-Circuit Board Layout Issues.....   | 425        |
| Approximate Inductance of a PC Board Trace Above a Ground Plane .....                          | 428        |
| Chapter 15 Problems.....   | 436        |
| References.....  | 437        |
| <b>Chapter 16: Other Useful Design Techniques and Loose Ends .....</b>                         | <b>439</b> |
| Thermal Circuits .....   | 439        |
| Steady-State Model of Conductive Heat Transfer .....   | 440        |
| Thermal Energy Storage .....   | 441        |
| Using Thermal Circuit Analogies to Determine Static Semiconductor<br>Junction Temperature..... | 444        |
| Mechanical Circuit Analogies.....  | 444        |
| The Translinear Principle.....   | 449        |
| Input Impedance of Infinitely Long Resistive Ladder .....                                      | 451        |
| Transmission Lines 101 .....   | 451        |
| Node Equations and Cramer's Rule.....  | 455        |
| Finding Oscillation Modes.....   | 458        |
| Some Comments on Scaling Laws in Nature .....  | 463        |
| Chapter 16 Problems.....   | 469        |
| References.....  | 472        |
| <b>Index .....</b>   | <b>475</b> |
| <b>What's on the CD-ROM?.....</b>  | <b>480</b> |



# Preface

What? Another textbook on analog circuit design? Well, this is not a textbook *per se*; rather, it is designed to be more of a design handbook for practicing engineers and students interested in learning more real-world techniques for designing and analyzing analog circuits using transistors, diodes, and operational amplifiers. The hope is that the reader will find a good mixture of theoretical techniques and also real-world design examples and test results.

This author is a practicing electrical engineer in the analog and power electronics realm who also has had the opportunity to teach at Worcester Polytechnic Institute.

The careful reader, upon review of the chapter references, will note that I have a fondness for using older references. This is due in part to the fact that the authors of these older texts and papers did not have computers available to them for circuit simulations and mathematical number-crunching. These references, in many cases, give very useful approximations, intuitive insights, and different ways of looking at difficult circuit analysis problems.

## Intended Audience

This text is loosely based on a set of course notes designed for my graduate-level analog circuit design seminar offered at Worcester Polytechnic Institute. Students who take my course have already taken undergraduate-level courses covering transistors, signal processing, Bode plots and the like. Furthermore, it is the author's hope that the techniques shown in the book will be useful for practicing analog (and perhaps even *digital!*) design engineers.

## Text Outline

Chapters 1 and 2 offer introductory material. Chapter 1 serves as an introduction and motivation to analog circuit design in general, with selected history thrown into the mix. Chapter 2 covers important signal-processing concepts that are used in later chapters, so that the reader will be on the "same page" as the author.

Chapters 3 to 8 cover the bipolar device physics, the bipolar junction transistor (BJT), transistor amplifiers, and approximation techniques for bandwidth estimation and switching speed analysis.

Chapter 9 covers the basics of CMOS and CMOS amplifiers. The bandwidth estimation techniques developed in earlier chapters for amplifier design work well for CMOS devices as well.

## **Preface**

---

Chapter 10 covers transistor switching. How do you get a transistor to turn ON and OFF quickly, and how do you estimate that speed?

Chapter 11 is a review of feedback systems and of the Bode plot/phase margin method of designing stable feedback systems.

Chapters 12–13 cover the design, use and limitations of real-world operational amplifiers, including voltage-feedback and current-feedback op-amps.

Chapter 14 covers the basics of analog low-pass filter design, including ladder and active implementations of Butterworth, Chebyshev, elliptic and Bessel filters.

Chapter 15 covers real-world design issues such as PC board layout rules-of-thumb and the use and limitations of passive components.

Chapter 16 is a potpourri of useful design techniques and tricks that don't fit into the other chapters.

Throughout the text, some illustrative analysis problems and MATLAB® and PSPICE design examples are haphazardly sprinkled.

## **Acknowledgments**

The author would like to acknowledge the learned professors and teaching assistants at the Massachusetts Institute of Technology who taught him many of the techniques shown in this book. They include Prof. Jim Roberge, Prof. Bill Siebert, Prof. Bill Peake, Prof. Marty Schlecht, Leo Casey, Tom Lee, Prof. Harry Lee, Prof. Campbell Searle, Prof. Amar Bose, and Prof. Dick Thornton.

This text has evolved from courses the author taught over the past years at Worcester Polytechnic Institute. Therefore, further thanks go to W.P.I. and its students and faculty who directly and indirectly contributed to this text. The author also acknowledges the indirect contributions of his W.P.I. students who, through their probing questions and careful reading of the course notes, have identified numerous typographical errors and half-truths, which hopefully have been fully expunged from this edition.

The author gratefully acknowledges the patience and technical support provided by the staff at Elsevier. The author also wishes to thank my friend and colleague Dr. Alexander Kusko, who reviewed the manuscript and offered many useful suggestions. Also thanks to my friend Dr. Jeff Roblee, who read the manuscript from a mechanical engineering point-of-view and offered many useful suggestions.

Plots were created using MATLAB and the Microsim Student Version of PSPICE, version 8.0.

**Marc T. Thompson**  
*Harvard Labs*  
*Harvard, Massachusetts*  
*October, 2005*