

# TIPS FOR DESIGNING HIGH-GAIN AMPLIFIERS

TRANSISTOR MODELS, ENGINEERING APPROXIMATIONS, AND GAIN AND BANDWIDTH CALCULATIONS HELP SIMPLIFY AMPLIFIER DESIGN.

Several techniques that emphasize intuition, not analytical results, can help simplify the design of a high-gain amplifier with wide bandwidth. This article takes a look these techniques, which include transistor models, gain and bandwidth calculations, and engineering approximations. The outcome is convincing—an augmented transistor model and

a few back-of-the-envelope calculations yield surprisingly predictable results. Also presented here is a practical example and a discussion of design strategy.

Suppose you need to design a transistor amplifier with  $-1000$  gain and a  $1$ -MHz,  $-3$ -dB bandwidth. An op amp isn't available, and you want to do the design with as few components as possible. An amplifier circuit is submitted for your approval (*Fig. 1a*). Will it do the job?

The small-signal network for this common-emitter amplifier is drawn using the standard transistor hybrid- $\pi$  model (*Fig. 1b*). The mid-band gain of this amplifier is:

$$\frac{v_{out}}{v_{in}} = -g_m R_L \frac{r_\pi}{R_s + r_x + r_\pi} \quad (1)$$


The gain of this amplifier approaches a theoretical maximum when  $R_s$  and  $r_x$  are small compared to  $r_\pi$ .

$$\frac{v_{out}}{v_{in}} \approx -g_m R_L \quad (2)$$

Equation 2 calculates the maximum gain achievable with one resistively-loaded gain stage. From transistor theory, we know that the transconductance of a transistor is linearly proportional to collector current:

$$g_m = \frac{I_c}{V_{TH}} \quad (3)$$

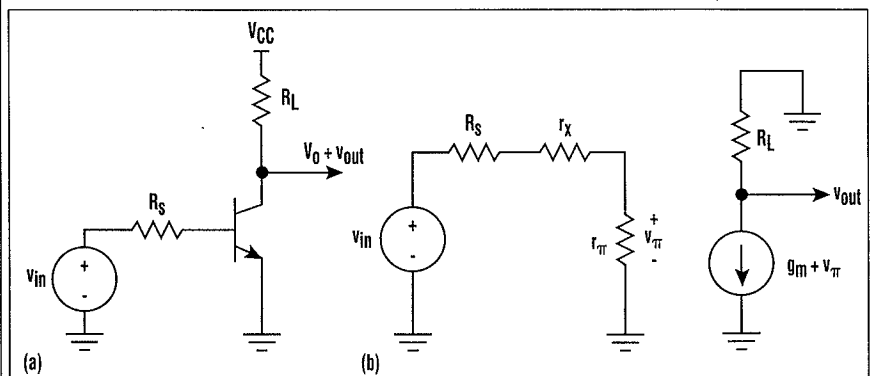MARC THOMPSON  
Polaroid Corp.,  
153 Needham St., Bldg. 1,  
Newton, MA 02164;  
(617) 386-4465.



**1. A RESISTIVELY-LOADED** common-emitter amplifier is used as a high-gain circuit (a). The small-signal network for this common-emitter amplifier is drawn using the standard transistor hybrid- $\pi$  model (b).

# DESIGN APPLICATIONS

## DESIGNING HIGH-GAIN AMPLIFIERS

where the transistor thermal voltage  $V_{TH} = kT/q \approx 25 \text{ mV}$  at room temperature. The small-signal gain is:

$$\frac{v_{out}}{v_{in}} \approx -\frac{I_C}{V_{TH}} R_L \quad (4)$$

For the transistor to stay biased in its linear region, the quiescent output voltage  $V_o$  must be higher than ground. The collector current of the transistor amplifier depends on power-supply voltage  $V_{CC}$  and quiescent output voltage:

$$I_C = \frac{V_{CC} - V_o}{R_L} \quad (5)$$

Finally, this gives a maximum theoretical gain of:


$$\frac{v_{out}}{v_{in}} \approx -\frac{(V_{CC} - V_o)}{V_{TH}} \quad (6)$$

For a supply voltage of 12 V and a small  $V_o$ , this transistor model shows that the small signal gain always will be less than 480. And if a reasonable output swing is desired, the gain will be significantly lower.

The simple hybrid- $\pi$  model used for this analysis indicates that the voltage gain of a resistively-loaded amplifier may be increased to  $\infty$  by increasing the power-supply voltage. Alternately, if the transistor is loaded with an ideal current source ( $R_L = \infty$ ), the model shows that we can get infinite voltage gain. But common sense prevails and a more detailed look at the inner workings of the transistor reveals that infinite gain is impossible. We then must modify the hybrid- $\pi$  model for high-gain circuits.
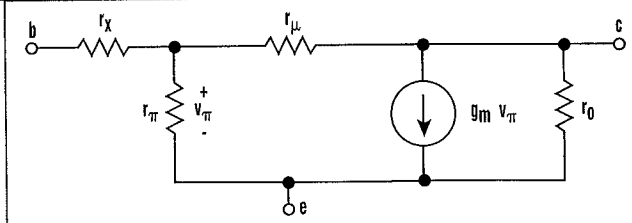
### DETAILED MODEL

The simple hybrid- $\pi$  model leads us to believe that transistor collector current doesn't change when collector voltage changes.<sup>1</sup> In other words, the simple model indicates infinite output impedance at a transistor's collector. Looking at an  $I_C$  versus  $V_{CE}$  trace on a transistor curve tracer dispels this



**2. MORE DETAIL** is given to the simple hybrid- $\pi$  transistor model by adding two more resistors to account for the effects of base-width modulation.

notion. James Early was the first to describe this effect, called base-width modulation.<sup>2</sup>

Base-width modulation causes both the collector current and base current of the transistor to change when the collector voltage changes. This also means that a transistor current source can't have infinite output impedance. The effect is modeled by adding two more resistors to the transistor model (Fig. 2). This augmented low-frequency model should be used when analyzing circuits with gains in excess of a few hundred.

The  $g_m$  and  $r_\pi$  for the extended model are the same as before:

$$g_m \approx \frac{I_C}{V_{TH}} \quad (7)$$

$$r_\pi = \frac{h_{fe}}{g_m} \quad (8)$$

As a result of base-width modulation, the output resistance of the transistor ( $r_o$ ) is inversely proportional to collector current.

$$r_o = \frac{1}{\eta g_m} \quad (9)$$

The proportionality constant  $\eta$  is what device physicists call the base-width modulation factor, which has typical values of  $10^{-3}$  to  $10^{-4}$ .

A change in collector voltage also affects base current. Changes in base current are a factor of  $h_{fe}$  smaller than changes in collector current. Therefore, the feedback resistance  $r_\mu$  is:

$$r_\mu = h_{fe} r_o \quad (10)$$

The picture gets clearer by plugging some real numbers into the equations. Using a curve tracer, the output resistance  $r_o$  and small-signal current gain  $h_{fe}$  of four 2N3904 and 2N3906 transistors were measured (surely not a scientific sampling, but who cares?). Other averaged parameters ( $r_\pi$ ,  $g_m$ ,  $r_\mu$ ) were calculated (Table 1). The averaged transistor-model values will be used to design a high-gain transistor amplifier.

### A DESIGN EXAMPLE

Consider the design of a one-gain-stage amplifier (Table 2). A common-emitter amplifier loaded with a current source will be designed using the measured transistor data (Fig. 3a).

$Q_1$  is the common-emitter amplifier, loaded with current-source transistor  $Q_2$ . The current source has a high output resistance, resulting in high gain from this one stage. The value of the input coupling capacitor is chosen  $C_c$  to meet the  $f_L$  specification.<sup>3</sup>  $Q_1$  and  $Q_2$  are biased at approximately 2.5 mA.

$Q_3$  buffers the output, and  $Q_4$  is a  $V_{BE}$ -multiplier providing a voltage drop of approximately  $8 V_{BE}$  so that the feedback loop will bias the transistors properly. Ignoring the loading effects of  $r_{\pi 1}$  on  $R_{in}$  and  $R_f$ , the amplifier's closed-loop gain is set by varying the potentiometer setting. Closed-loop gain is approximately given by:

$$\frac{v_{out}}{v_{in}} \approx -\frac{R_f}{R_{in}} \quad (11)$$

This gain equation is exactly like that of an inverting op-amp gain stage. In order for the amplifier to behave like an "ideal" amplifier, and for the gain equation to hold true, the amplifier's open-loop gain must be much larger than 1000. So, let's figure out the open-loop gain (Fig. 3b).

Several approximations can be made when calculating open-loop gain. First,  $r_\pi > R_{in}$ , so the transistor's

**TABLE 1: AVERAGE TRANSISTOR PARAMETERS**

Transistor	$I_C$	$r_\pi$	$g_m$	$r_o$	$h_{fe}$	$r_\mu$
2N3904	5 mA	1 k $\Omega$	0.2 mho	75 k $\Omega$	200	15 M $\Omega$
2N3906	5 mA	875 $\Omega$	0.2 mho	27 k $\Omega$	175	4.7 M $\Omega$

**TABLE 2: DESIGN SPECIFICATIONS**

Transistors	2N3904, 2N3906
Gain	> 1000
$f_L$ (low-frequency -3-dB point)	< 500 Hz
$f_H$ (high-frequency -3-dB point)	> 1 MHz
Power dissipation	< 100 mW
Power-supply voltages	+12, -12

**DESIGN APPLICATIONS**  
**DESIGNING HIGH-GAIN AMPLIFIERS**

**TABLE 3: TRANSISTOR SMALL-SIGNAL PARAMETERS**

Transistor	$I_c$	$g_m$	$r_\pi$	$r_o$	$r_\mu$	$C_\pi$	$C_\mu$
Q <sub>1</sub>	2.5 mA	0.1	2 kΩ	150 kΩ	30 MΩ	50 pF	2 pF
Q <sub>2</sub>	2.5 mA	0.1	1.75 kΩ	54 kΩ	9.4 MΩ	50 pF	4 pF
Q <sub>3</sub>	1.5 mA	0.06	3.33 kΩ	250 kΩ	50 MΩ	30 pF	2 pF
Q <sub>5</sub>	2.5 mA	0.1	2 kΩ	150 kΩ	30 MΩ	50 pF	3 pF

**TABLE 4: TRY 1—CURRENT-SOURCE-LOADED COMMON-EMITTER AMPLIFIER**

Parameter	Spice results	Prototype measurements
Closed-loop gain	1070	1050
$f_L$	180 Hz	190 Hz
$f_H$	220 kHz	400 kHz
Output swing	5 V p-p	5 V p-p
Power dissipation	70 mW	75 mW

input impedance won't load down the input that much. Second, the effective resistance due to feedback is  $R_f / (\text{open-loop gain})$ . This is also much smaller than  $R_{in}$ . The current-source transistor  $Q_2$  is replaced by an equivalent resistance  $r_{out2}$  looking into the collector of  $Q_2$ . (We'll figure out real numbers later.) The emitter follower is replaced by an equivalent input resistance  $r_{in3}$  looking into the base of  $Q_3$ . Furthermore, the gain of the emitter follower will be close to 1, and won't be calculated here. The amplifier's open-loop gain is solved by summing currents at the output node:

$$g_{m1}V_{in} + \frac{V_{out}}{r_{o1} \parallel r_{out2} \parallel r_{in3}} + \frac{V_{out} - V_{in}}{r_{\mu 1}} = 0 \quad (12)$$

By grouping terms, and making the

approximations:

$$g_{m1} \gg \frac{1}{r_{\mu 1}}, r_{\mu 1} \gg r_{o1} \quad (13)$$

we arrive at the final answer:

$$\frac{V_{out}}{V_{in}} (\text{open loop}) \approx -g_{m1} (r_{o1} \parallel r_{out2} \parallel r_{in3}) \quad (14)$$

This is similar to the gain equation for the resistively-loaded common-emitter amplifier, except that in this case the load resistance at the output node has been made quite large by using a current source. Also, we can't ignore the input impedance of the emitter follower and the output resistance of  $Q_1$ . Going by the data in Table 1, we know that  $r_{o1}$  for  $Q_1$  is approximately 150 kΩ, because  $r_o$  is inversely proportional to collector current, and

$Q_1$  is biased at 2.5 mA. We still need to calculate the output resistance of the  $Q_2$  current source  $r_{out2}$ , and the input resistance  $r_{in3}$  of the  $Q_3$  emitter follower.

$Q_1$  and  $Q_2$  are biased at 2.5 mA, with  $Q_3$  biased at approximately 1.5 mA. The  $f_T$  for the 2N3904 and 2N3906 transistors is about 300 MHz. Each transistor has a base-spreading resistance  $r_x \approx 150 \Omega$  at this bias level. The  $C_\pi$  of each transistor is calculated by:

$$C_\pi \approx \frac{g_m}{2\pi f_T} - C_\mu \quad (15)$$

$C_\mu$  for each transistor is a few picofarads, and depends somewhat on the collector-base voltage. Small-signal parameters can be calculated for these bias levels (Table 3).

We'll use a small-signal model to

### THE MILLER APPROXIMATION

The Miller approximation is a useful way to think about high-gain amplifiers. For the common-emitter amplifier, consider the small-signal model (see the figure, a). The amplifier is driven by a voltage source with source resistance  $R'_s$ , which may include the base-spreading resistance  $r_x$  of the transistor. Capacitance at node  $v_a$  may be modeled as  $C_\pi$  in parallel with some other elements. Then, the mid-band gain is:

$$\frac{V_{out}}{V_a} \approx -g_m R_L \quad (B1)$$

The feedback around  $C_\mu$  can be modeled with  $a_v = g_m R_L$  as the gain from base to collector (see the figure, b). The capacitance looking to the right of  $C_\pi$  is the so-called Miller capacitance. Miller capacitance is found by applying a test-voltage source to the  $v_a$  node, and finding the test current.

$$C_M = (1 + a_v)C_\mu \quad (B2)$$

Total capacitance at node  $v_a$  is the sum of the Miller capacitance  $C_M$


with the intrinsic transistor capacitance  $C_\pi$ .

$$C_{in} \approx C_\pi + (1 + a_v)C_\mu \quad (B3)$$


For a high-gain amplifier ( $g_m R_L$  is large), the input capacitance is often dominated by the Miller capacitance, which is proportional to amplifier gain. In this high-gain case, the bandwidth of the amplifier is approximately given by the following equation:

$$\omega_h \approx \frac{1}{(R'_s \parallel r_x)C_{in}} \quad (B4)$$

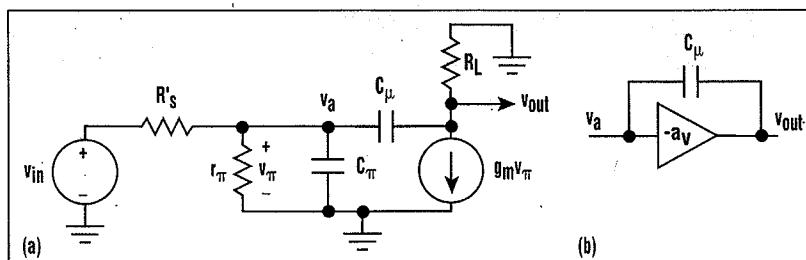An exact analysis shows that the Miller-effect approximation is equivalent to calculating the dominant pole of the amplifier and ignoring other poles. In many cases, amplifier poles are widely spaced with one dominant pole, so it turns out that the approximation is a very good one.



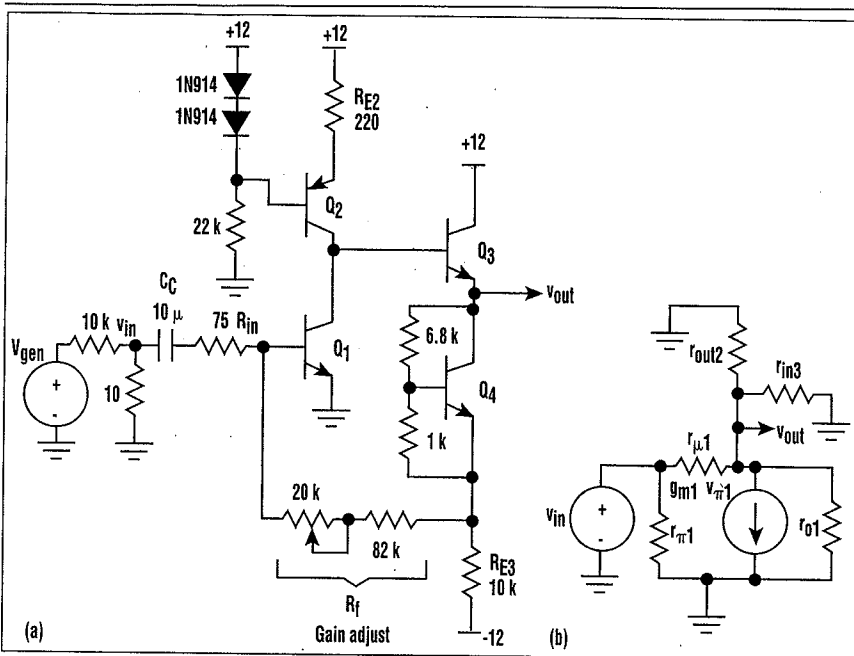DESIGN APPLICATIONS  
**DESIGNING HIGH-GAIN AMPLIFIERS**



**3. A ONE-GAIN-STAGE** common-emitter amplifier loaded with a current source is designed using the measured transistor data (a). The amplifier's open-loop gain is calculated from the circuit's small-signal model (b).

find the output resistance of the current source  $Q_2$  (Fig. 4a). A simplifying approximation is to ignore  $r_{x2}$  (which is small compared to  $r_{\pi 2}$ ) and the resistance of the diode string that's biasing  $Q_2$ 's base (which is also small). To find this output resistance, add a test-voltage source  $V_T$ , and calculate the resulting current  $I_T$ .

At first, this circuit looks complicated, but it can be simplified to ease the calculation. It's clear from Figure 4 that the resistance at the collector of  $Q_2$  is  $r_{\mu 2}$  in parallel with a bunch of other elements. Let's omit  $r_{\mu 2}$  and add it in later. We'll first find the output resistance of the modified circuit (Fig. 4b).

Because the entire test current flows through the  $r_{\pi}R_{E2}$  combination, the voltage  $v_{\pi 2}$  is found by:

$$v_{\pi 2} = -I_T(r_{\pi 2} \parallel R_{E2}) \quad (16)$$

where  $R_{E2}$  is the 220-Ω resistor at the emitter of  $Q_2$ . Solving for the test current:

$$I_T = \frac{V_T + v_{\pi 2}}{r_{o2}} + g_{m2}v_{\pi 2}$$

$$= \frac{V_T - I_T(r_{\pi 2} \parallel R_{E2})}{r_{o2}} + g_{m2}I_T(r_{\pi 2} \parallel R_{E2}) \quad (17)$$

Recognizing that  $g_{m2} > 1/r_{o2}$ , this reduces to:


$$I_T(1 + g_{m2}(r_{\pi 2} \parallel R_{E2})) \approx \frac{V_T}{r_o} \quad (18)$$

Now, adding in the  $r_{\mu 2}$ , which we previously omitted, results in:

$$r_{out2} \approx r_{\mu 2} \parallel r_o(1 + g_{m2}(r_{\pi 2} \parallel R_{E2})) \quad (19)$$

**TABLE 5: TRY 2—CURRENT-SOURCE-LOADED COMMON-EMITTER AMPLIFIER (WITH CASCODE)**

Parameter	Spice results	Prototype measurements
Gain	1110	1100
$f_L$	180 Hz	190 Hz
$f_H$	1.1 MHz	1.3 MHz

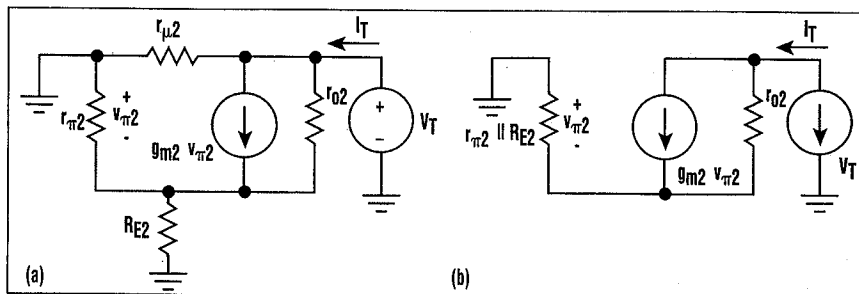

**4. THE SMALL-SIGNAL MODEL** of the current source  $Q_2$  is used to find its output resistance (a). At first this circuit looks complicated, but it's possible to simplify it by omitting  $r_{\mu 2}$  (b).

The output resistance of the current source is made larger if there's an emitter resistor. Therefore, the 220-Ω resistor in our circuit helps to increase the current source output resistance. If  $R_E > r_{\pi}$ , the output resistance approaches  $r_{\mu}/2$ , which is a very large value. At the bias levels chosen, component values are  $g_{m2} = 0.1$ ,  $r_{\pi 2} = 1750 \Omega$ ,  $r_{o2} = 54 \text{ k}\Omega$ , and  $r_{\mu 2} = 9.4 \text{ M}\Omega$ . The output resistance  $r_{out2} \approx 900 \text{ k}\Omega$ .

The final step is to find the input resistance of the emitter follower (Fig. 5). The resistance looking into the base of  $Q_3$  (the derivation of which is left as an exercise for the reader) is given by:

$$r_{in3} = r_{\mu 3} \parallel \{ (r_{\pi 3} + (1 + h_{fe3})(r_{o3} \parallel R_{E3})) \} \quad (20)$$

With  $R_{E3} = 10 \text{ k}\Omega$ ,  $Q_3$  is biased at approximately 1.5 mA, resulting in:  $g_{m3} = 0.06$ ,  $r_{\pi 3} = 3.3 \text{ k}\Omega$ ,  $r_{o3} = 250 \text{ k}\Omega$ , and  $r_{\mu 3} = 50 \text{ M}\Omega$ . This results in  $r_{in3} \approx 2 \text{ M}\Omega$ .

Because  $r_{o1}$  is the smallest of the three resistors at the output node, it's the limiting factor in the amplifier's open-loop gain. The sum of the three equivalent resistors in parallel results in a resistance of approximately 114 kΩ between the high-gain node and ground. From Equation 14, the open-loop gain is approximately -11,400. This gain is high enough so that when the loop is closed, the amplifier's gain should approach the ideal gain.

If the gain is now acceptable, what about the bandwidth? If we assume that there's one dominant pole (that pole being due to the Miller capacitance of  $Q_1$ ), and that all other poles are at frequencies much higher than 1 MHz, the gain-bandwidth product of the amplifier will be constant. In order for our amplifier with closed-loop gain

DESIGN APPLICATIONS  
**DESIGNING HIGH-GAIN AMPLIFIERS**

of -1000 to have a -3-dB bandwidth of 1 MHz, the open-loop bandwidth must be at least 90 kHz (at a gain of 11,400). The dominant pole of this amplifier is due to the effective source resistance ( $R_{in} + r_{x1}$ ) interacting with the Miller capacitance (see "The Miller approximation," p. 86). Other poles (for instance, in the emitter follower  $Q_3$ ) will be at much higher frequencies. This can be seen by applying the method of Open-Circuit Time Constants to the amplifier.<sup>4,5</sup> Using the Miller approximation, and assuming  $a_v = 11,400$ ,  $C_{\mu1} = 2$  pF,  $r_{\pi1} = 2$  k $\Omega$ ,  $r_{x1} = 150$   $\Omega$ , and  $R_{in} = 85$   $\Omega$ , the open-loop -3-dB bandwidth is given by:


$$f_H \approx \frac{1}{2\pi((R_{in} + r_{x1}) \| r_{\pi1}) a_v C_{\mu1}} \approx 33 \text{ kHz} \quad (21)$$

The Miller approximation tells us that at a gain of 1000, the closed loop bandwidth won't be much larger than 380 kHz. Measurements on the breadboard prototype and Spice results confirm this prognosis (Table 4). The Miller effect is killing us!


What can be done to squeeze more bandwidth out of the circuit? Because the Miller effect is hurting us, let's overcome it by using a cascode transistor (Fig. 6). With the added cascode transistor  $Q_5$ , the gain at the collector of  $Q_1$  is low because transistor  $Q_5$  has a small output resistance at its emitter. This defeats the Miller effect by isolating the high gain node from the input transistor  $Q_1$ . The input capacitance of  $Q_1$  is now much lower (approximately  $C_{\pi1} + 2C_{\mu1}$ ), moving the input pole up to a frequency given by:

$$f_{\text{input\_pole}} \approx \frac{1}{2\pi(r_{\pi1} \| (R_{in} + r_{x1})) (C_{\pi1} + 2C_{\mu1})} \approx 14 \text{ MHz} \quad (22)$$

This amplifier's dominant time con-

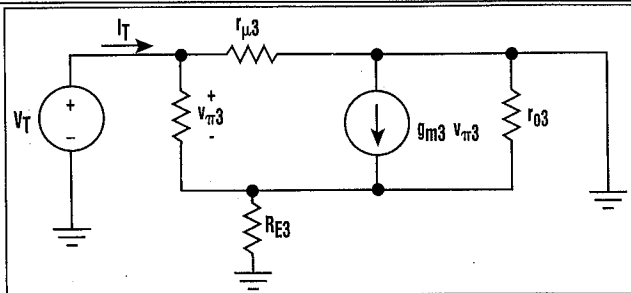

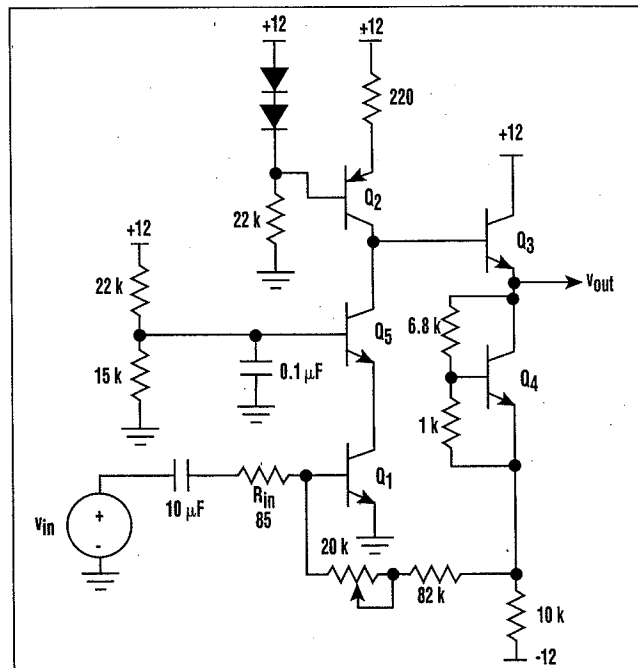**5. ENGINEERS CAN** calculate the input resistance of the emitter follower using the circuit's small-signal model.



**6. ADDING A CASCODE** transistor will eradicate the Miller effect and squeeze more bandwidth out of the single-stage high-gain amplifier circuit.

stant will be the resistance of the high-gain node (now higher than 114 k $\Omega$ , due to the cascode transistor) interacting with the various capacitances at the node. All other poles will be at frequencies much higher than our closed-loop bandwidth of 1 MHz. The modified circuit also will have a higher open-loop gain, because the cascode transistor reduces the effects of base-width modulation on transistor  $Q_1$ .

Now, let's do a non-rigorous, seat-of-the-pants calculation. Because  $Q_5$  has a high impedance at its emitter, the output resistance at the collector of the cascode transistor will be approximately  $r_{\mu5}/2$  (see Equation 18). Consequently, the equivalent resistance  $r_{eq}$  at the high-gain node now is approximately equal to the output re-

sistance of the current source  $r_{out2}$  in parallel with the input resistance of the emitter follower. This resistance  $r_{eq} \approx 600$  k $\Omega$ . Therefore, the open-loop gain ( $\approx -g_{m1} r_{eq}$ )  $\approx -60,000$ .

$C_{\mu2}$  will be slightly larger than in the previous circuit, because  $V_{CB2}$  is smaller with the added cascode transistor. There's no Miller effect, so the total capacitance  $C_T$  at the high-gain node is approximately  $C_T = C_{\mu5} + C_{\mu2} + C_{\mu3} + \text{stray capacitances} \approx 10$  pF. Given this, the dominant open-loop pole is approximately:

$$f_{OL} \approx \frac{1}{2\pi r_{eq} C_T} \approx 26 \text{ kHz} \quad (23)$$

The poles are widely spaced, so the feedback loop should be stable and with a bandwidth 60 times larger than the dominant open-loop pole  $\approx 1.6$  MHz. We expect the actual bandwidth to be lower, and measurements show that it is, due to other unexplained effects (Table 5).

Finally, the bandwidth specifications have been met. This article demonstrates that it's possible to design a simple, high-gain amplifier with wide bandwidth. To reiterate, the approach used was designed to emphasize intuition, not analytical results.  $\square$

*Marc Thompson is a senior engineer at Polaroid's Medical Imaging Systems, where he specializes in high-speed analog design. He has two patents for the design of high-speed, high-power laser diode modulators. Marc holds a BSEE and MSEE from the Massachusetts Institute of Technology, Cambridge, and is currently on a leave-of-absence from Polaroid pursuing his PhD at MIT.*



*This article is fourth in a series of Marc's analog design articles that have run in Electronic Design over the past year. The four articles are based on his analog-design seminar that's offered at Polaroid.*


References:

1. Roberge, James K., *Operational Amplifiers: Theory and Practice*,


# MICRO-T OSCILLATORS SLASH SPACE

for greater computing power.

 They take up only 5 x 7mm. Yet our new T series surface-mount crystal oscillators can drive "full-size" loads – 50 pF HCMOS or 10 TTL – at frequencies ranging from 1.8 MHz through 66.7 MHz. So they're ideal for the latest PCMCIA cards, or any application where board space is at a premium but maximum performance is paramount. 

Hermetically sealed at 420°C, our Micro-T's are the state of the art in full-load oscillators – and the smallest. We make them right here, so you won't have long to wait for delivery. You'll like our prices, too. 

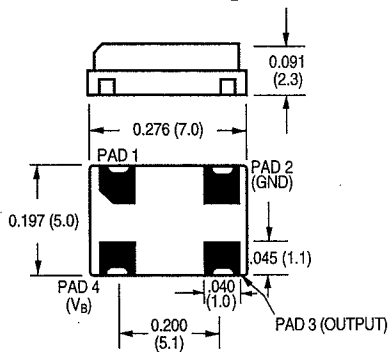To find out more, call or write MF Electronics Corp.



Model	Type	Stability	Operating Temperature	Input Voltage
T1280	Fixed	.01%	0 to 70°C	5V ± 0.5V
T1282	Fixed	.005%	0 to 70°C	5V ± 0.5V
T1258	Fixed	.01%	-40 to +85°C	5V ± 0.5V
T3290	Tristate	.01%	0 to 70°C	5V ± 0.5V
T3292	Tristate	.005%	0 to 70°C	5V ± 0.5V
T3258	Tristate	.01%	-40 to +85°C	5V ± 0.5V

**MF Electronics**  
COMPONENTS THAT SET THE PACE  
10 Commerce Dr. • New Rochelle, NY 10801  
(914) 576-6570 • FAX: (914) 576-6204

## DESIGN APPLICATIONS DESIGNING HIGH-GAIN AMPLIFIERS

John Wiley and Sons: New York, 1975, p. 309-326.

2. Early, James, "Effects of Space-Charge Layer Widening in Junction Transistors," Proceedings of the I.R.E., November 1952, p. 1401-1406.

3. Thompson, Marc, "SCTC Analysis Estimates Low-Frequency -3-dB Point," *Electronic Design*, October 1, 1993, p. 65-68.

4. Thompson, Marc, "Design Linear Circuits Using OCTC Calculations," *Electronic Design Special Analog Issue*, June 24, 1993, p. 41-47.

5. Thompson, Marc, "Network Tricks Aid in OCTC," *Electronic Design*, December 16, 1993, p. 67-70.

HOW VALUABLE?	CIRCLE
HIGHLY	553
MODERATELY	554
SLIGHTLY	555

## "YOUR FREE CATALOG KNOCKED MY SOCKS OFF"

We get that sort of comment all the time. People are impressed that our free Consumer Information Catalog lists so many free and low-cost government booklets. There are more than 200 in all, containing a wealth of valuable information.


Our free Catalog will very likely impress you, too. But first you have to get it. Just send your name and address to:

**Consumer Information Center  
Department KO  
Pueblo,  
Colorado  
81009**



A public service of this publication and the Consumer Information Center of the U. S. General Services Administration

## EXCESS INVENTORY IS CHANGING HIS LIFE

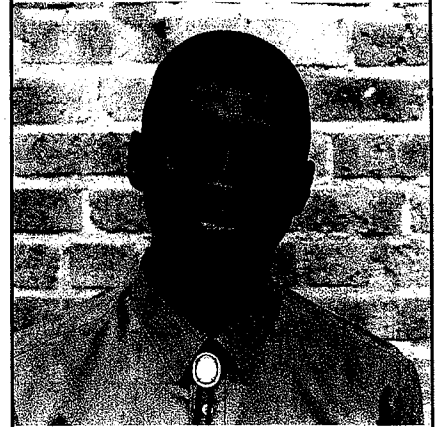

Anthoine has the chance to break the vicious cycle of poverty which strangles his neighborhood. Up until now his best "career" opportunity would be gangs and drugs.

That was before EAL.

Even though he's still in 8th grade, Anthoine knows there's a college scholarship waiting for him. EAL's "Excess Inventory for Scholarships" program is giving him the hope and incentive he needs to finish high school.

If your company has excess inventory, you can change a life by donating it to EAL.

For More Details  
Call 708-690-0010  
Peter Roskam  
Executive Director

 **EAL**  
Educational Assistance Ltd., Inc.  
P.O. Box 3021  
GLEN ELLYN, ILLINOIS 60138